

Verilog Manual

PART B (Using Xilinx Vivado tool)

5. Write a Verilog code and implement Adders & Subtractors.
6. Design Comparators.
7. Realize SR, JK, T & D Flip-Flops.
8. Design Counters & Shift Registers.
9. Design Clock Pulse Generator.
10. Design and implement 4-bit ALU using Verilog program.

Write a Verilog code and implement Adders & Subtractors.

Aim:


1. Model in Verilog for a 1-bit half adder.
2. Model in Verilog for a full adder and add functionality to perform logical operations of XOR, XNOR, AND, and OR gates. Write a test bench with appropriate input patterns to verify the modeled behaviour.

Software Required:


Xilinx Vivado

1-bit Half Adder

Block Diagram:

 

Logic Diagram:

 

Truth table:

| INPUT | | OUTPUT | |
|-------|---|--------|-------|
| a | b | sum | carry |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

BOOLEAN EXPRESSIONS:

$\text{out_sum} = a \oplus b$

$\text{out_carry} = a \cdot b$

CODE:

Dataflow:

```
module half_adder(sum,carry,a,b);
    input a,b;
    output sum,carry;
    assign sum=a^b;
    assign carry= a & b;
endmodule
```

Testbench Code

```
module half_adder_tb();
    reg a,b;
    wire sum,carry;
    half_adder U2(sum,carry,a,b);
    initial
```


```

begin
    a=1'b0; b = 1'b0;
#5 a=1'b0; b = 1'b1;
#5 a=1'b1; b = 1'b0;
#5 a=1'b1; b = 1'b1;
#5
$finish;
end
endmodule


```

Full Adder

Block Diagram:

 

Logic Diagram:

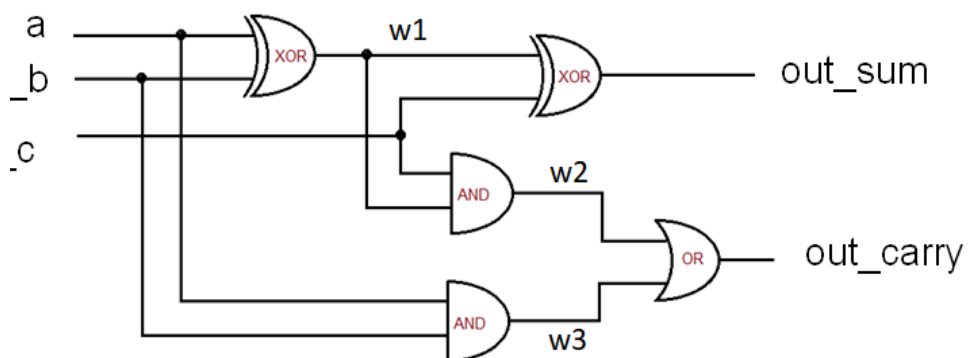

Truth table:

| INPUT | | | OUTPUT | |
|-------|----|----|--------|-------|
| in | in | in | sum | carry |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

BOOLEAN EXPRESSIONS:

$\text{sum} = a \oplus b \oplus c$

$\text{carry} = ab + bc + ca$

CODE:

Dataflow:

```
module full_adder (out_sum, out_carry, in_a, in_b, in_c);
module full_adder(sum,carry,a,b,c);
input a,b,c;
output sum,carry;
assign sum=a^b^c;
assign carry=(a & b) | (a & c) | (b & c);
endmodule
```

Testbench Code

```
module full_adder_tb();
reg a,b,c;
wire sum,carry;
full_adder U5(sum,carry,a,b,c);
initial
begin
a=1'b0;
b = 1'b0;
c =1'b0;
#5 c =1'b1;
#5 b=1'b1; c=1'b0;


#5 c=1'b1;
```

```

#5 a=1'b1;b=1'b0;c=1'b0;
#5 c=1'b1;
#5 b=1'b1; c=1'b0;
#5 c=1'b1;
#5
$finish;
end
endmodule

```

EXPECTED WAVEFORM:

 

Realize SR, JK, T & D Flip-Flops.

Aim:

Simulation and realization of following Flip Flop


- D Flip Flop
- JK Flip Flop
- SR Flip Flop

Software Required:

Xilinx Vivado

A. D Flip Flop

Block Diagram:

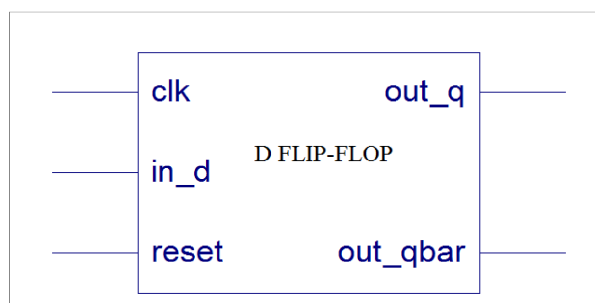

Truth table:

| INPUT | | | OUTPUT | |
|-------|-------|------|-----------|----------|
| clk | reset | in_d | out_q | out_qbar |
| ↑ | 0 | 0 | 0 | 1 |
| ↑ | 0 | 1 | 1 | 0 |
| ↑ | 1 | X | 0 | 1 |
| ↓ | X | X | No change | |

CODE:**Behavioural:**

```


module d_ff (clk, reset, in_d, out_q, out_qbar);
    input clk, reset, in_d;
    output out_q, out_qbar;
    reg out_q;
    always @ (posedge clk or posedge reset)
begin
    if(reset)
        out_q <= 1'b0;
    else
        out_q <= in_d;
    end
    assign out_qbar = ~out_q;
endmodule

```

Testbench code:


```
module d_fftest;
    reg clk;
    reg reset;
    reg in_d;
    wire out_q;
    wire out_qbar;
    d_ff d1 (.clk(clk), .reset(reset),.in_d(in_d),.out_q(out_q),.out_qbar(out_qbar));
    initial
    begin
        clk = 1'b0;
        forever
            #5 clk=~clk;
    end
    initial
    begin
        $display("Time | clk | reset | in_d | out_q | out_qbar ");
        $monitor("%4d | %3b | %5b | %3b | %6b | %7b |",
        $time, clk, reset, in_d, out_q,out_qbar);
        reset = 1'b1; in_d = 1'b1;
        #10;
        reset =1'b0;
        in_d=1'b0;
        #10; in_d= 1'b1;
        #10; $finish;
    end
endmodule
```

EXPECTED WAVEFORM:

 

B. JK Flip Flop

Block Diagram:

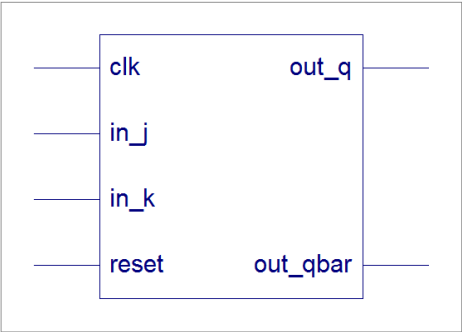

Truth table:

| INPUT | | | | OUTPUT | |
|-------|-------|------|------|-------------|----------|
| clk | reset | in_j | in_k | out_q | Out_qbar |
| ↑ | 0 | 0 | 0 | (No change) | |
| ↑ | 0 | 0 | 1 | 0 | 1 |
| ↑ | 0 | 1 | 0 | 1 | 0 |
| ↑ | 0 | 1 | 1 | Toggles | |
| ↑ | 1 | X | X | 0 | 1 |

CODE:**Behavioural:**

```
module jk_ff (clk, reset, in_j, in_k, out_q, out_qbar);
    input clk, reset, in_j, in_k;
    output out_q, out_qbar;
    reg out_q;
    always @(posedge clk or posedge reset)
        begin
            if(reset)
                out_q<=1'b0;
            else
                begin
                    case ({in_j, in_k})
                        2'b00: out_q<=out_q;
                        2'b01: out_q<=1'b0;
                        2'b10: out_q<=1'b1;
                        2'b11: out_q<=~out_q;
                        default: out_q<=out_q;
                    endcase
                end
            end
        assign out_qbar=~out_q;
    endmodule
```

Testbench code:

```
module jk_ff_tb;
    reg clk;
```

```

reg reset;
reg in_j;
reg in_k;
wire out_q;
wire out_qbar;

jk_ff jk1(.clk(clk), .reset(reset), .in_j(in_j), .in_k(in_k), .out_q(out_q),
.out_qbar(out_qbar));
initial
begin
    clk=1'b0;
    forever
        #5 clk= ~clk;
end
initial
begin
$display("Time | clk | reset | in_j | in_k| out_q | out_qbar ");
$monitor("%4d | %3b | %5b | %3b | %3b| %6b| %7b|",
$time, clk, reset, in_j, in_k, out_q,out_qbar);
    reset=1'b1;
#10;
reset=1'b0;
    in_j=1'b0;
    in_k=1'b0;
#10;
    in_k=1'b1;
#10;
    in_j=1'b1;
    in_k=1'b0;
#10;
    in_k=1'b1;

```

```

    #10;
$finish;
end
endmodule


```

EXPECTED WAVEFORM:



C. SR Flip Flop

Block Diagram:

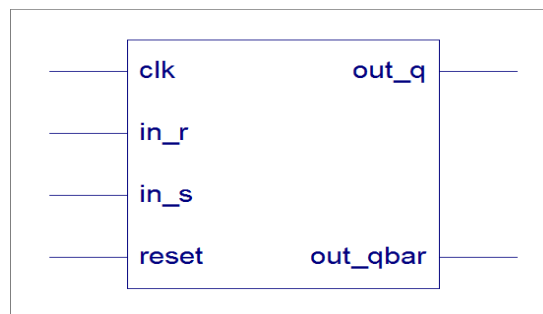

Truth table:

| INPUT | | | | OUTPUT | |
|-------|-------|------|------|-------------|----------|
| clk | reset | in_s | in_r | out_q | Out_qbar |
| clk | 0 | 0 | 0 | (No change) | |
| ↑ | 0 | 0 | 1 | 0 | 1 |
| ↑ | 0 | 1 | 0 | 1 | 0 |
| ↑ | 0 | 1 | 1 | X (Invalid) | |
| ↑ | 1 | X | X | 0 | 1 |
| ↑ | | | | | |

CODE:**Behavioural:**

```
module sr_ff (clk,reset,in_s,in_r, out_q,out_qbar);
input clk, reset, in_s, in_r;
output out_q, out_qbar;
reg out_q;
always @(posedge clk or posedge reset)
begin
if(reset)
out_q<=1'b0;
else
begin
case({in_s, in_r})
2'b00:out_q<=out_q;
2'b01:out_q<=1'b0;
2'b10:out_q<=1'b1;
2'b11:out_q<=1'bx;
default:out_q<=out_q;
endcase
end
end
assign out_qbar = ~out_q;
endmodule
```

Testbench code:


```
module sr_ff_tb();
reg clk, reset, in_s, in_r;
wire out_q, out_qbar;
```

```

sr_ff sr1 (.clk(clk), .reset(reset), .in_s(in_s), .in_r(in_r), .out_q(out_q),
.out_qbar(out_qbar));
initial
begin
clk=1'b0;
forever
#5 clk= ~clk;
end
initial
begin
$display("Time | clk | reset | in_s | in_r | out_q | out_qbar ");
$monitor("%4d | %3d | %5d | %b | %b | %b | %b |",
$time,clk, reset, in_s, in_r, out_q,out_qbar);
reset=1'b0;
in_s=1'b0;
in_r=1'b0;
#10;
reset=1'b1;
#10;
reset=1'b0;
#10;
in_r=1'b1;
#10;
in_s=1'b1;
in_r=1'b0;
#10;
in_r=1'b1;
#10 $finish;
end
endmodule

```

EXPECTED WAVEFORM:

 

Design and implement 4-bit ALU using Verilog program.

Aim:

Simulation and realization of 4-bit ALU

Software Required:

Xilinx Vivado

Block Diagram:

Basic Operation based on 3-bit opcode

| Op-code | ALU Operation |
|---------|----------------|
| 000 | $A + B$ |
| 001 | $A - B$ |
| 010 | Increment by 1 |

| | |
|-----|-----------------|
| 011 | Decrement by 1 |
| 100 | True |
| 101 | Ones complement |
| 110 | AND operation |
| 111 | OR operation |

CODE:

Dataflow:

```

module alu4 (in_a, in_b, c_opcode, o_result);
input [3:0] in_a, in_b;
input [2:0] c_opcode;
output [3:0] o_result;
reg [3:0] o_result;
always@(in_a, in_b, c_opcode)
begin
case (c_opcode)
3'b000: o_result = in_a + in_b;
3'b001: o_result = in_a - in_b;
3'b010: o_result = in_a + 1;
3'b011: o_result = in_a - 1;
3'b100: o_result = in_a?1:0; // true
3'b101: o_result = ~in_a; // Complement
3'b110: o_result = in_a & in_a; //AND Bitwise
3'b111: o_result = in_a | in_a; // OR Bitwise
default : o_result = 32'bx;
endcase
end

```

```
endmodule
```

Test bench code:

```
module alu4_tb;
  reg [3:0] in_a, in_b;
  reg [2:0] c_opcode;
  wire [3:0] o_result; integer i;
  alu32 U0 (in_a, in_b, c_opcode, o_result);
  initial
  begin
    $display("| Time | in_a | in_b | c_opcode | o_result |");
    $monitor("%4d | %4d | %4d | %3d | %8d", $time, in_a, in_b, c_opcode, o_result);
    in_a = 10;
    in_b = 4;
    c_opcode = 0;
    for (i = 0; i < 8; i = i+1)
      #5 c_opcode = i;
    #5
    $finish;
  end
endmodule
```

EXPECTED WAVEFORM:

OUTPUT:

Design Counters & Shift Registers.

Aim:


Simulation and realization of 4-bit binary and BCD synchronous counters

Software Required:

Xilinx Vivado

A. 4-bit Synchronous Binary Counter:

Block Diagram:

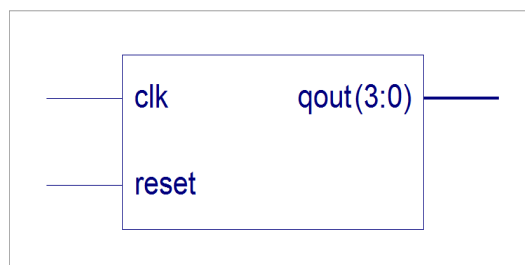

Truth table:

| Clk | Reset | Present State | | | | Next State | | | |
|-----|-------|---------------|-------|-------|-------|------------|-------|-------|-------|
| | | qout3 | qout2 | qout1 | qout0 | qout3 | qout2 | qout1 | qout0 |
| ↑ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| ↑ | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| ↑ | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| ↑ | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| ↑ | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |

Up Counter:

CODE:

Behavioural:

```
module binary_sync_up (clk, reset, qout);  
    input clk;  
    input reset;  
    output [3:0] qout;  
    reg [3:0] qout;  
    always @ (posedge clk)  
    begin  
        if(reset)  
            qout <= 4'b0000;  
        else  
            qout <= qout+1;  
        end  
    endmodule
```

Testbench code:

```
module binary_Sync_up_tb();  
    reg clk;  
    reg reset;  
    wire [3:0] qout;  
    binary_sync_up u0 (.clk(clk),.reset(reset),.qout(qout));  
    initial  
    begin  
        clk=1'b0;  
        forever
```


```

        #10 clk=~clk;
end

initial
begin
    reset=1'b1;
    #30;
    reset=1'b0;
    #200;
    reset=1'b1;
    #10;
    reset=1'b0;
#350;
    $finish;
end
endmodule

```

EXPECTED WAVEFORM:

 

Down Counter:

CODE:

Behavioural:

```

module binary_sync_down (clk, reset, qout);
    input clk;
    input reset;
    output [3:0] qout;
    reg [3:0] qout;

```

```

always @ (posedge clk)
begin
    if(reset)
        qout <= 4'b0000;
    else if
        (qout == 4'b0000)
        qout = 4'b1111;
    else
        qout <= qout-1;
    end
endmodule

```


Testbench code:

```

module binary_Sync_down_tb();
    reg clk;
    reg reset;
    wire [3:0] qout;
    binary_sync_down u0 (.clk(clk),.reset(reset),.qout(qout));
    initial
    begin
        clk=1'b0;
        forever
            #10 clk=~clk;
    end
    initial
    begin
        reset=1'b1;
        #30;
        reset=1'b0;
        #200;
        reset=1'b1;
        #10;
        reset=1'b0;
        #350;
        $finish;
    end
endmodule


```

EXPECTED WAVEFORM:

 

B. 4-bit BCD Synchronous Counter

Block Diagram:

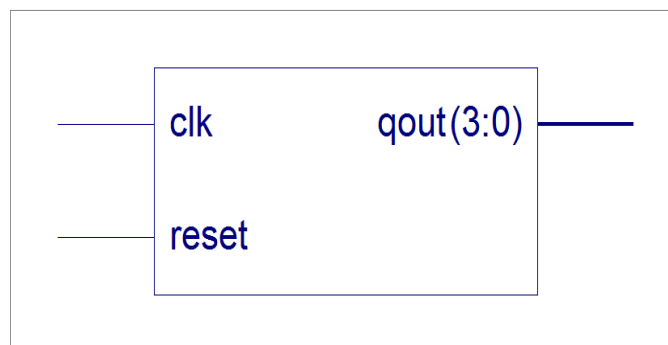

Truth table:

| Clk | Reset | Present State | | | | Next State | | | |
|-----|-------|---------------|-------|-------|-------|------------|-------|-------|-------|
| | | qout3 | qout2 | qout1 | qout0 | qout3 | qout2 | qout1 | qout0 |
| ↑ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| ↑ | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| ↑ | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| ↑ | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| ↑ | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| ↑ | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| ↑ | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| ↑ | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| ↑ | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| ↑ | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |

Up Counter:

CODE:

Behavioural:

```
module BCDsyn_up (reset, clk, qout);
input clk;
input reset;
output [3:0] qout;
reg [3:0] qout=4'b0000;
always@(posedge clk)
begin
if(reset==1)
qout =4'b0000;
else if (qout>=4'b1001)
qout =4'b0000;
else
qout = qout+1;
end
endmodule
```

Testbench code:


```
module BCD_Sync_up_tb( );
reg clk;
reg reset;
wire [3:0] qout;
BCDsyn_up u0 (.clk(clk),.reset(reset),.qout(qout));
initial
begin
clk=1'b0;
forever
#10 clk=~clk;
```

```

end
initial
begin
    reset=1'b1;
    #30;
    reset=1'b0;
    #200;
    reset=1'b1;
    #10;
    reset=1'b0;
#350;
    $finish;
end
endmodule

```

EXPECTED WAVEFORM:

 

Down Counter:

CODE:

Behavioural:

```

module BCDsyn_down (reset, clk, qout);
input clk;
input reset;
output[3:0] qout;
reg [3:0]qout=4'b0000;
always@(posedge clk)

```

```

begin
    if(reset==1)
qout=4'b0000;
    else if (qout<=4'b0000)
qout =4'b1001;
    else
qout = qout-1;
end
endmodule

```

Testbench code:

```

module BCD_sync_down();
    reg clk;
    reg reset;
    wire [3:0] qout;
BCDsyn_down u0 (.clk(clk),.reset(reset),.qout(qout));
initial
begin
    clk=1'b0;
    forever
        #10 clk=~clk;
end
initial
begin
reset=1'b1;
    #30;

reset=1'b0;
    #200;
    reset=1'b1;
    #10;

```



```

        reset=1'b0;
#350;
    $finish;
end
endmodule

```

EXPECTED WAVEFORM:

